



Faculty of Engineering and Technology
Electrical and Computer Engineering Department Computer
Architecture ENCS4370

Project #2

design and verify a simple RISC processor in Verilog

Prepared by:

Ibaa Taleeb	1203073
Sewar AbuEid	1200043
Rahaf Naser	1201319

Instructor: Dr.Ayman Hroub

Section: 1

Date: 18-01-2024

Table of Contents

1.Designs and Testing for Stages	4
1.1 Instruction Memory	4
1.2 MUX 2X1	5
1.3 MUX 4X1	5
1.4 Register File	5
1.5 PC Register	Error! Bookmark not defined.
1.6 Data Memory	6
1.7 Arithmetic Logic Unit (ALU).....	6
1.8 Extender 16	7
1.9 control unit.....	7
1.10 Registers.....	7
1.11 Stack And Stack Pointer (SP)	8
2.Control Signals Table	9
3. Expressions for Control Bits	11
4. The Finite State Machine	12
5.Final Data path	14
5.1. Final Data path simulation	15
6. Conclusion	19
7.Appendices	20
7.1. The Code for the data Path	20
7.2. The Test Bench For The System.....	43

List of Figures

Figure 1:Instruction Memory	4
Figure 2: Program counter	4
Figure 3:Mux 2x1.....	5
Figure 4:mux 4x1.....	5
Figure 5:Register File.....	6
Figure 6: Data Memory	6
Figure 7: ALU	7

1.Designs and Testing for Stages

1.1 Instruction Memory

The Instruction Memory, also known as the Instruction Cache, is an essential element within the data path of a computer system. Its primary function is to store and supply instructions for execution, facilitating swift access and efficient processing. Instruction Memory plays a pivotal role in the execution of programs.

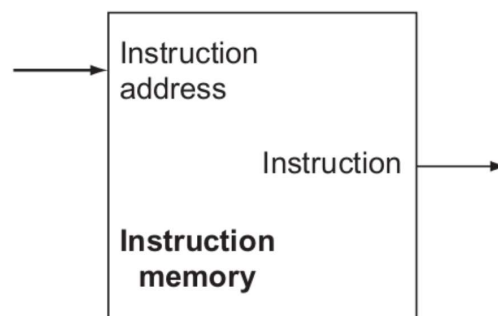


Figure 1:Instruction Memory

1.2 Program Counter

A PC (program counter) processor has a register that holds the address of the subsequent instruction that needs to be run from memory. It is also known as the instruction address register (IAR), instruction counter, and instruction pointer. It is a 16-bit register. A PC, also known as a program counter, is a digital counter used to track the current execution point and complete operations rapidly. . It retains the memory address of the subsequent instruction slated for fetching and execution. As a fundamental aspect of control flow, the PC Register dictates the sequence of instructions and undergoes updates during the fetch stage. This functionality enables the execution of branching and jumping instructions, facilitating alterations in the control flow within the program. In essence, the PC Register is instrumental in overseeing the orderly execution flow of the program.

 


Figure 2: Program counter

1.3 MUX 2X1

The 2x1 MUX, or a 2-to-1 multiplexer, is a frequently utilized component in the data path of a computer system. function involves choosing one input signal from a pair based on a select signal. Within the data path, it is frequently employed for operations such as data selection and routing. By enabling the selection of diverse data sources through control signals, it enhances the flexibility and functionality of the data path.

 


Figure 3: Mux 2x1

1.3 MUX 4X1

The 4x1 MUX, also known as a 4-to-1 multiplexer, is a frequently utilized component in the data path of a computer system. Its primary role involves the selection of one input signal from a set of four, determined by a select signal. Within the data path, it finds application in activities like instruction decoding and accessing the register file. This multiplexer facilitates signal selection and routing, thereby enhancing the flexibility and functionality of the data path.

 


Figure 4: mux 4x1

1.4 Register File

The register file comprises a collection of registers employed to temporarily store data between memory and the functional units. It also includes the circuits responsible for writing to and reading from these registers. Additionally, the inputs and outputs of the register file, encompassing destination and source registers, have already been configured.

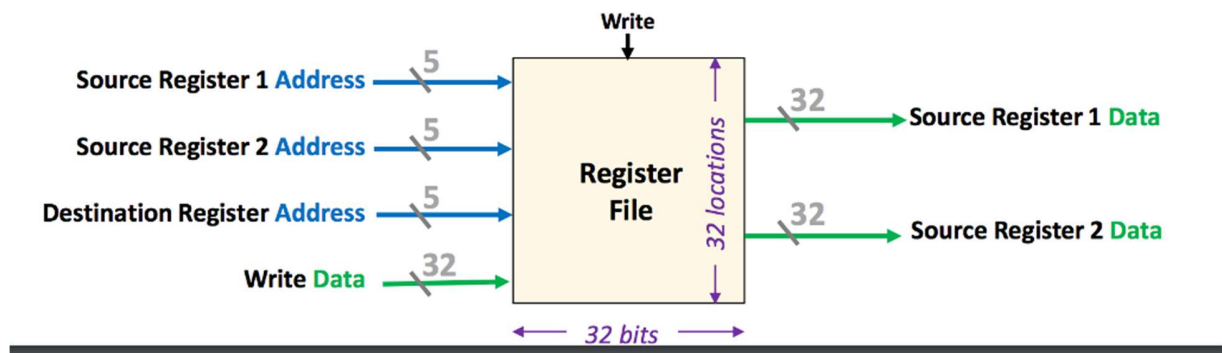


Figure 5: Register File

1.6 Data Memory

The Data Memory stage is a crucial component in the data path of a computer system. It facilitates the reading and writing of data to and from the main memory. During this stage, data is transferred between the processor and memory subsystem. Operations such as fetching data, storing data, and performing necessary conversions are performed. The Data Memory stage plays a vital role in executing instructions that involve memory operations, ensuring correct data access and manipulation. In this program the memory is organized into three segments:

- Static data segment
- Code segment
- Stack segment

 


Figure 6: Data Memory

1.7 Arithmetic Logic Unit (ALU)

The Arithmetic Logic Unit (ALU) is like the brain center of a computer's main processor. Its main job is to handle all the math and logic tasks with binary numbers. So, it can add, subtract, multiply, divide, and compare numbers. This is super important because it allows the computer to do all kinds of calculations

and decision-making. When a computer is following instructions, the ALU kicks into action during a stage where it does the necessary math or logic stuff for each task. The Zero Flag

 


Figure 7: ALU

1.8 Extender 16

Extender 16 plays a vital role in the data path when there is a requirement to expand the size of a data signal by 16 bits. It guarantees compatibility in data size, performs sign extension, aligns with broader data paths, and facilitates expanded range or precision in operations. The inclusion of the Extender 14 ensures that the data path can effortlessly manage larger data sizes, preserve sign integrity, and support intricate calculations, thereby improving overall efficiency and precision in data processing.

1.9 control unit

The control unit is a pivotal component within the data path of a computer system. It makes sure all the parts work together smoothly by telling them what to do. It manages things like processing data, using memory, and dealing with input/output. It reads and understands instructions from the program counter, then guides the different parts like the ALU, registers, and memory to do their jobs correctly. Basically, the control unit is the leader, making sure the computer follows the plan and works well.


1.10 Registers

The Register, serving as a buffer between stages, holds significant importance in a multi-cycle data path for several crucial reasons. Firstly, it facilitates the synchronization of operations. In a multi-cycle setup, different stages carry out operations in distinct clock cycles. The Register ensures a smooth flow of data between stages by allowing each stage to complete its operation before passing the data to the next one. This synchronization guarantees that each stage receives accurate data at the appropriate time. Additionally, the Register plays a vital role in timing control, helping regulate the timing of data propagation between stages. This control ensures the proper sequencing of operations, preventing issues like data hazards or corruption. By providing a controlled and synchronized transfer of data, it maintains the integrity of the overall process. Moreover, the Register serves as a storage element for intermediate results generated at various

stages in a multi-cycle data path. This preservation of intermediate results allows for effective data dependency management and ensures the correct flow of data through the entire data path.

 1.11 Stack And Stack Pointer (SP)

In this computer system, there's a 32-bit special purpose register known as the Stack Pointer (SP), and it's crucial for managing the stack. The stack is a Last In First Out (LIFO) data structure, meaning the last item added is the first one to be removed. The SP keeps track of the topmost empty element in the stack. As a programmer, you can see and manipulate this register.. The Stack segment is particularly important as it holds information like return addresses and registers' values during function calls. The system provides explicit instructions for the programmer to push or pop elements onto or from the stack, allowing for efficient management of data and control flow in the program.



2.Control Signals Table

num	inst	Op1	PcCont	Ext	Alusrc	AluOP	M.rd	M.Wr	MemAdd	DataIn	W.port1	W.port2	Wb.data	SPorAlu2	Alup
1	and	000000	00	x	00	01	0	0	x	x	1	0	0	x	X
2	add	000001	00	x	00	00	0	0	x	x	1	0	0	x	x
3	sub	000010	00	x	00	10	0	0	x	x	1	0	0	x	X
4	andi	000011	00	0	01	01	0	0	x	x	1	0	0	x	X
5	addi	000100	00	0	01	00	0	0	x	x	1	0	0	x	X
6	Lw	000101	00	1	01	00	1	0	0	x	1	0	1	x	X
7	Lw.poi	000110	00	1	01	00	1	0	0	x	1	1	1	x	X
8	Sw	000111	00	1	01	00	0	1	0	0	0	0	x	x	X
9	Bgt	001000	01	1	10	10	0	0	x	x	0	0	x	x	X
10	Blt	001001	01	1	10	10	0	0	x	x	0	0	x	x	X
11	Beq	001010	01	1	10	10	0	0	x	x	0	0	x	x	X
12	Bne	001011	01	1	10	10	0	0	X	x	0	0	x	x	X
13	Jmp	001100	10	x	x	x	0	0	x	x	0	0	x	x	X
14	Call	001101	10	x	x	x	0	0	1	1	0	0	x	1	0
15	Ret	001110	11	x	x	x	0	0	x	x	0	0	x	0	1
16	Push	001111	00	x	x	x	0	1	1	0	0	0	x	1	x
17	pop	010000	00	x	x	x	1	0	1	1	0	0	1	0	1

- PcCount :
 00 \Rightarrow pc=pc+1
 01 \Rightarrow pc=pc+sign_ext(imm16)
 10 \Rightarrow pc=contactx
 11 \Rightarrow pc=top of the stack
- ALU src :
 00 \Rightarrow Rs2
 01 \Rightarrow extendedImm(16bit)
 10 \Rightarrow Rd
- ALUop:
 00 \Rightarrow add
 01 \Rightarrow and
 10 \Rightarrow sub

- AluOp2
0 → add 1
1 → sub
- SPorALU
0 → SP
1 → SP added or subset by 1
- Ext
0 → unsigned
1 → signed
- Wport 1 → Rd (To enable writing the value of Rd on the register file)
- Wport 2 → Rs1 (To enable writing the value of Rs1 on the register file)
- Wb data
0 → result from Alu
1 → from memory
- Data in
0 → rd
1 → pc+1
- MemAddress
0 → alu result
1 → result of mux SporAlu

3. Expressions for Control Bits

- `pcCount[0] : (instruction==Jmp)&(instruction==Call)&(instruction==Ret)`
- `pcCount[1]:(instruction==Bgt)&(instruction==Bltn)&(instruction==Beq)&(instruction==Bne) &(instruction==Ret)`
- `Ext: (instruction==lw)&(instruction==lw.poi)&(instruction==Sw)&(instruction==Bgt)&(instruction==Bne)&(instruction==Bltn)&(instruction==Beq)`
- `Alusrc[0]:`
`(instruction==Bgt)&(instruction==Bltn)&(instruction==Beq)&(instruction==Bne)`
- `Alusrc[1]:(instruction==andi)&(instruction==addi)&(instruction==lw)&(instruction==lw.poi)&(instruction==Sw)`
- `AluOP[0]:(instruction==sub)&(instruction==Bgt)&(instruction==Bltn)&(instruction==Beq)&(instruction==Bne)`
- `AluOP[1]: (instruction==and)& (instruction==andi)`
- `M.rd: (instruction==lw)&(instruction==lw.poi)& (instruction==pop)`
- `M.Wr: (instruction==Sw)& (instruction==push)`
- `MemAdd: (instruction==Call)&(instruction==push) & (instruction==pop)`
- `DataIn: (instruction==Call)& (instruction==pop)`
- `W.port1:(instruction==R-type) &(instruction==andi) &(instruction==addi) &(instruction==lw) &(instruction==lw.poi)`
- `W.port2: (instruction==lw.poi)`
- `Wb.data: (instruction==lw)&(instruction==lw.poi)& (instruction==pop)`
- `SPorAlu2: (instruction==Call)&(instruction==push)`
- `AluSp: (instruction==Ret)&(instruction==pop)`

4. The Finite State Machine

Here are the stages are the states in which:

- **Instruction Fetch:** The processor fetches the instruction from memory and loads it into the instruction register.
- **Instruction Decode:** The processor decodes the instruction, determines the type of instruction and the operands needed, and stores the relevant information in internal registers.
- **Execution:** The processor performs the necessary operations, which may involve multiple clock cycles, to complete the instruction.
- **Memory Access:** If the instruction requires data to be read from or written to memory, the processor accesses the memory to perform the operation.
- **Write Back:** The processor writes the result of the operation back to the appropriate internal register or memory location.

The finite state machine below shows the transition between stages from fetch to write back and the behavior of each instruction respectively.


 


Figure1:Finite State Machine


The table of control unit shows the corresponding value to control signal and instruction implemented. While the figure above shows the transition per instruction, for example 'and, add, sub' instructions being fetch decoded executed and write back to register file then return to fetch state for the next instruction, while 'j' is being fetched decoded and then return to fetch again.

5. Final Data path

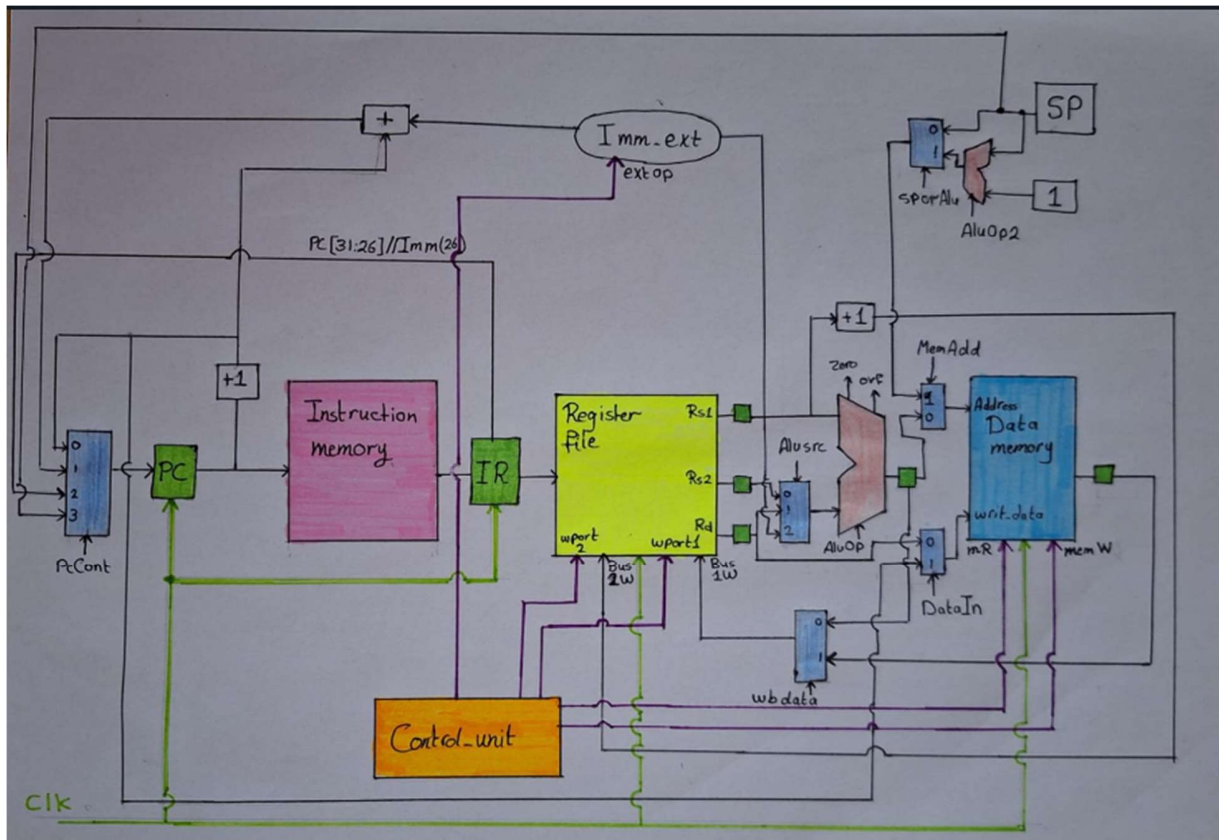


Test Each Instruction

→ AND instruction Simulation

 


The result in Rd is (00000001) which is the and result of (00000001) & (00000005).

→ ADD instruction Simulation

 


Note that the content of Rd as a result is 0000002D which equals 45 which is the summation of 31 (0000001F) and 14 (0000000E).


→SUB instruction Simulation

 


→ANDI instruction Simulation

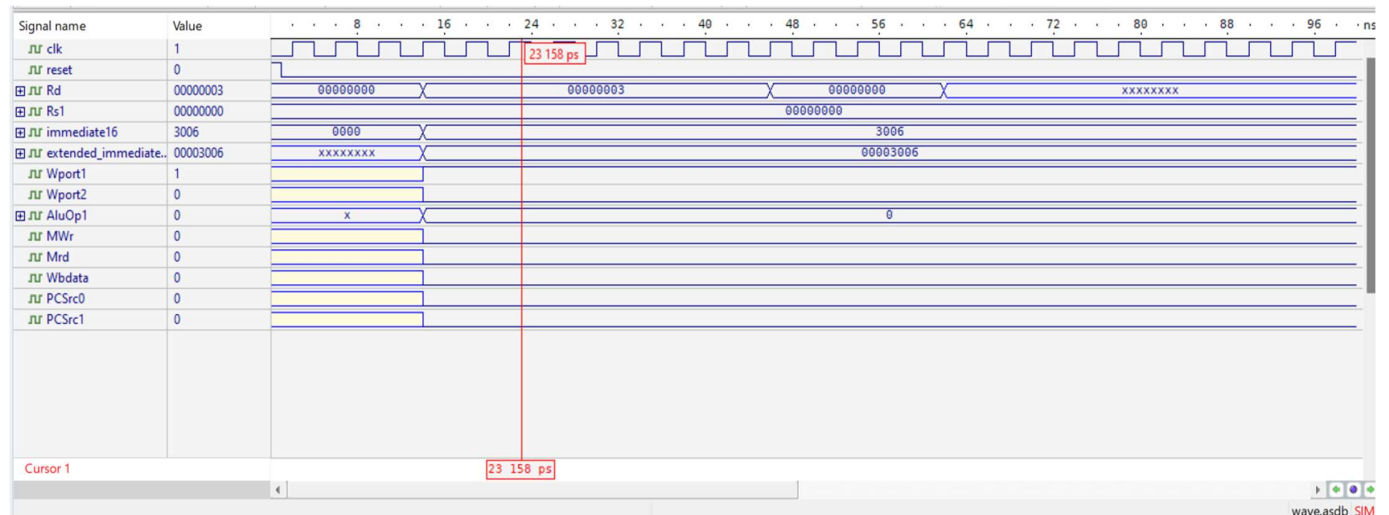

→ADDI instruction Simulation

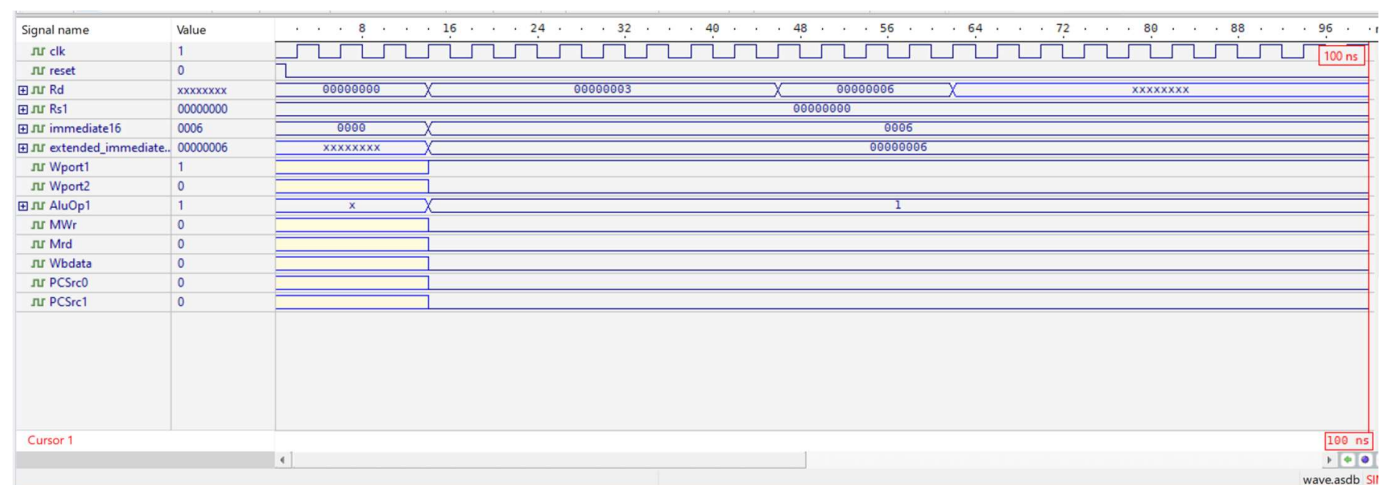


➔LW instruction Simulation

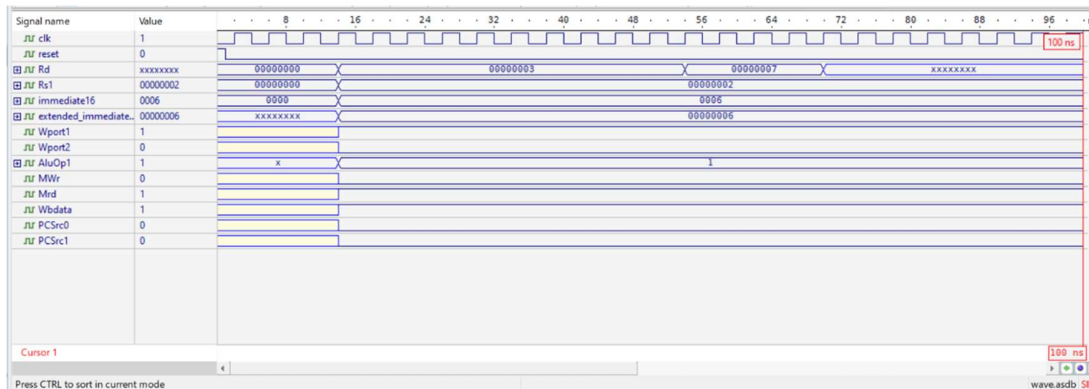


➔LW.POI



➔SW instruction simulation

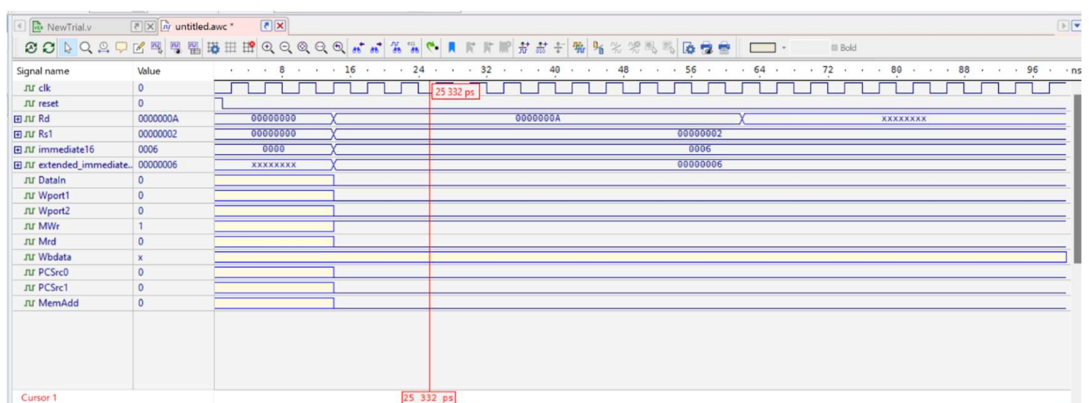

Final Data Path testing

 

6. Conclusion

The project involved demonstrating the complete construction of the data path based on specified instructions. Each stage was developed with the necessary control signals to regulate their operations. A simulation was performed for every step, along with the design work for creating the required data path and the final state machine, all of which are detailed in the report.

7. Appendices

7.1. The Code for the data Path

```
// the first step is to define the global variables outside the module

reg [2:0]current_state; // 0--> Instruction Fetch 1--> Instruction Decode 2-->Execution 3--> Memory
access 4--> Write Back Data

reg [2:0]next_state; // takes the same range of values of the current_state
reg [31:0]IR; // ISA of 32-bit


module multiCycleProcessor( // determine the control signals
input clk,input reset,
output reg [1:0] PcCont,output reg ExtOp,
output reg      Wport1,
output reg  Wport2,output reg Alusrc,output reg [1:0] AluOp1,
output reg MemAdd,output reg DataIn,output reg  Mrd,
output reg  MWr, output reg Wbdata , output reg SPorAlu2,
output reg AluSpOp,

///Instruction Decode Part
output reg [31:0] Rs1, // (Bus A )Output data from register 1
output reg [31:0] Rs2, // (Bus B) Output data from register 2
output reg [31:0] Rd, // (Bus W) Output data from register 3

///ALU Part
output reg [31:0] outputOfALU, // Just to verify that the ALU works properly
///immediate16 Part
output reg [31:0]extended_immediate16,
///immediate26 Part
```

```
);
```

```
// variables will be used in the instruction fetch stage
```

```
reg [31:0] InstMem [0:31]; // bit width of each element in the array (InstMem) is 32-bit
```

```
//and The range [31:0] indicates that the least significant bit (LSB) is 0, and the most significant bit (MSB) is 31.
```

```
reg [31:0] PC;
```

```
reg [31:0] SP;
```

```
reg [5:0] OpCode1;
```

```
// Decode Stage
```

```
reg [31:0] mux_2Output;
```

```
reg [31:0] toRegFile; // the data will be stored in the register file
```

```
reg [3:0] RegisterFile[0:31]; // 16 Registers 32-bit each
```

```
reg [3:0] RdAddress; // Address for Rd
```

```
reg [3:0] Rs1Address; // Address for RS1
```

```
reg [3:0] Rs2Address; // Address for RS2
```

```
reg [31:0] PCmuxOut; // the decided value of the PC
```

```
reg [31:0] sequentialPC ;
```

```
reg [31:0] jumpTargetAddress;
```

```
reg [31:0] branchTargetAddress;
```

```
// Alu Part
```

```
reg [31:0] firstOperand;
```

```
reg [31:0] secondOperand;
```

```
reg zero;
```

```
reg overflow;
```

```
// Memory access part
```

```

reg [31:0] address,data_in;    // data_in represent the data itself which will enter the memory not the
selection                    the same for address

reg [31:0] secondAddress,SPfinalResult; // this represent the output value of the SP mux

reg [31:0] data_out;

reg [31:0] data_memory [31:0];


//Extenders 16 and 26

reg [15:0] immediate16;

reg [25:0] immediate26;


// Stack Pointer Part


reg [31:0] SP_AlarResult; // increment or decrement the SP
reg [31:0] out_SP_mux; // to select either sp or alu result


// variable i for the loop
reg [7:0] i; // Example declaration for an 8-bit register "i"


initial
    begin
        InstMem[0]= 32'h14854000;//LW
        InstMem[1]= 32'h04890000;//ADD
        InstMem[2]= 32'h01980000;//AND
        InstMem[3]= 32'h2998C000;//BEQ
        InstMem[4]= 32'h3D800000;//PUSH
        InstMem[5]= 32'h18048001;//LW.POI
        InstMem[6]= 32'h40800000;//POP
        InstMem[7]= 32'h09288000;//SUB
        InstMem[8]= 32'hC4480000;//BGT
    end

```

```

        InstMem[9]= 32'h0C000000;//ANDI
        InstMem[10]= 32'h10440000;//ADDI
        InstMem[11]= 32'h1C518000;//SW
        InstMem[12]= 32'h0489C000;//BLT
        InstMem[13]= 32'h34000028;//JMP
        InstMem[14]= 32'h2D88000C;//CALL
        InstMem[15]= 32'h2E98C000;//BNE
        InstMem[16]= 32'h38000000;//RET

    end

    // adapt the clk setting to move between states
    always @(posedge clk)
case (current_state)
0:
    next_state = 1;
1:
    next_state = 2;
2:
    next_state = 3;
3:
    next_state = 4;
4:
    next_state = 0;
endcase

    // change the current state to it's next at each clk      positive edge
    always @(posedge clk)
current_state = next_state;

```

```

always @(posedge clk, posedge reset)
if (reset)
    begin
        current_state = 4;
        PC = 32'h00000000;
        Rs1 = 32'd0;
        Rs2 = 32'd0;
        Rd = 32'd0;
        mux_2Output = 32'h00000000;
        for (i = 0; i < 31; i = i + 1)
            RegisterFile[i] <= 32'h00000000;
    end

////////// Start Instruction tour Bismillah //////////

    else if (current_state == 0) begin
//instruction fetch
IR = InstMem[PC]; // the current instruction is the value of PC
OpCode1 = IR[31:26]; // the 6 MSB from IR always for the opcode

if (OpCode1 == 6'b000000) begin ///AND

            PcCont = 2'b00;
            Alusrc = 2'b00;
            AluOp1 = 2'b01;
            Mrd = 1'b0;
            MWr = 1'b0;
            Wport1 = 1'b1;

```



```

        Wport2 = 1'b0;
        Wbdata = 1'b0;

end

else if (OpCode1 == 6'b000001) begin//ADD
        PcCont = 2'b00;
        Alusrc = 2'b00;
        AluOp1 = 2'b00;
        Mrd = 1'b0;
        MWr = 1'b0;
        Wport1 = 1'b1;
        Wport2 = 1'b0;
        Wbdata = 1'b0;

end

else if (OpCode1 == 6'b000010) begin    //SUB

        PcCont = 2'b00;
        Alusrc = 2'b00;
        AluOp1 = 2'b10;
        Mrd = 1'b0;
        MWr = 1'b0;
        Wport1 = 1'b1;
        Wport2 = 1'b0;
        Wbdata = 1'b0;

end

```

```
else if (OpCode1== 6'b000011) begin    //ANDI
```

```
    PcCont = 2'b00;
```

```
    ExtOp = 1'b0;
```

```
    Alusrc = 2'b01;
```

```
    AluOp1 = 2'b01;
```

```
    Mrd = 1'b0;
```

```
    MWr = 1'b0;
```

```
    Wport1 = 1'b1;
```

```
    Wport2 = 1'b0;
```

```
    Wbdata = 1'b0;
```

```
end
```

```
else if (OpCode1 == 6'b000100) begin    //ADDI
```

```
    PcCont = 2'b00;
```

```
    ExtOp = 1'b0;
```

```
    Alusrc = 2'b01;
```

```
    AluOp1 = 2'b00;
```

```
    Mrd = 1'b0;
```

```
    MWr = 1'b0;
```

```
    Wport1 = 1'b1;
```

```
    Wport2 = 1'b0;
```

```
    Wbdata = 1'b0;
```

```
end
```

```
else if (OpCode1 == 6'b000101) begin //LW
```

```
    PcCont = 2'b00;  
    ExtOp = 1'b1;  
    Alusrc = 2'b01;  
    AluOp1 = 2'b00;  
    Mrd = 1'b1;  
    MWr = 1'b0;  
    MemAdd= 1'b0;  
    Wport1 = 1'b1;  
    Wport2 = 1'b0;  
    Wbdata = 1'b1;
```

```
end
```

```
else if (OpCode1 == 6'b000110) begin //LW.POI
```

```
    PcCont = 2'b00;  
    ExtOp = 1'b1;  
    Alusrc = 2'b01;  
    AluOp1 = 2'b00;  
    Mrd = 1'b1;  
    MWr = 1'b0;  
    MemAdd= 1'b0;  
    Wport1 = 1'b1;  
    Wport2 = 1'b1;  
    Wbdata = 1'b1;
```

```
end
```

```
else if (OpCode1 == 6'b000111) begin //SW
```

```
    PcCont = 2'b00;
```

```
    ExtOp = 1'b1;
```

```
    Alusrc = 2'b01;
```

```
    AluOp1 = 2'b00;
```

```
    Mrd = 1'b0;
```

```
    MWr = 1'b1;
```

```
    MemAdd= 1'b0;
```

```
    DataIn = 1'b0;
```

```
    Wport1 = 1'b0;
```

```
    Wport2 = 1'b0;
```

```
end
```

```
else if (OpCode1 == 6'b001000) begin //BGT
```

```
    PcCont = 2'b01;
```

```
    ExtOp = 1'b1;
```

```
    Alusrc = 2'b10;
```

```
    AluOp1 = 2'b10;
```

```
    Mrd = 1'b0;
```

```
    MWr = 1'b0;
```

```
    Wport1 = 1'b0;
```

```
    Wport2 = 1'b0;
```

```
end
```

```
else if (OpCode1 == 6'b001001) begin //BLT
```

```
    PcCont = 2'b01;
```

```

        ExtOp = 1'b1;
        Alusrc = 2'b10;
        AluOp1 = 2'b10;
        Mrd = 1'b0;
    MWr = 1'b0;
        Wport1 = 1'b0;
        Wport2 = 1'b0;

end

else if (OpCode1 == 6'b001010)begin    //BEQ
        PcCont = 2'b01;
        ExtOp = 1'b1;
        Alusrc = 2'b10;
        AluOp1 = 2'b10;
        Mrd = 1'b0;
    MWr = 1'b0;
        Wport1 = 1'b0;
        Wport2 = 1'b0;

end

else if (OpCode1 == 6'b001011) begin //BNE
        PcCont = 2'b01;
        ExtOp = 1'b1;
        Alusrc = 2'b10;
        AluOp1 = 2'b10;
        Mrd = 1'b0;

    MWr = 1'b0;

```

```

        Wport1 = 1'b0;
        Wport2 = 1'b0;

end

else if (OpCode1 == 6'b001100) begin //JMP
        PcCont = 2'b01;
        Mrd = 1'b0;
        MWr = 1'b0;
        Wport1 = 1'b0;
        Wport2 = 1'b0;
end

else if (OpCode1 == 6'b001101) begin //CALL
        PcCont = 2'b01;
        Mrd = 1'b0;
        MWr = 1'b0;
        MemAdd= 1'b1;
        DataIn = 1'b1;
        Wport1 = 1'b0;
        Wport2 = 1'b0;
        SPorAlu2= 1'b1;
        AluSpOp = 1'b0;
end

else if (OpCode1 == 6'b001110)begin //RET
        PcCont = 2'b11;
        Mrd = 1'b0;
        MWr = 1'b0;

```

```

        Wport1 = 1'b0;
        Wport2 = 1'b0;
        SPorAlu2= 1'b0;
        AluSpOp = 1'b1;
end

else if (OpCode1 == 6'b001111) begin //PUSH
        PcCont = 2'b00;
        Mrd = 1'b0;
        MWr = 1'b1;
        MemAdd= 1'b1;
        DataIn =1'b0;
        Wport1 = 1'b0;
        Wport2 = 1'b0;
        SPorAlu2= 1'b1;

end

else if (OpCode1 == 6'b010000) begin //POP
        PcCont = 2'b00;
        Mrd = 1'b1;
        MWr = 1'b0;
        MemAdd= 1'b1;
        DataIn =1'b1;
        Wport1 = 1'b0;
        Wport2 = 1'b0;
        Wbdata = 1'b1;
        SPorAlu2= 1'b0;
        AluSpOp = 1'b1;

```

end

end // the end of Instruction Fetch stage

else if (current_state == 1) begin

 // Instruction Decode stage

 // get the values of the extended and unextended immediates

immediate16 = IR[29:14];

// initially extend the value of immediate16 to 32-bit with zero's temporarily

extended_immediate16 = {16'b0000000000000000, immediate16}; // temporarily zero extension

immediate26 = IR[31:6]; // This value will not be extended

// here, we will fill the registers as needed

RegisterFile[1]=32'h00000003; // R1=3

RegisterFile[3]=32'h00000004; // R3=4

RegisterFile[4]=32'h0000000E; // R4=10

RegisterFile[5]=32'h00000007; // R5=7

RegisterFile[8]=32'h00000000; // R8=0

RegisterFile[9]=32'h00000001; // R9=1

///Getting the addresses for the RS1,RS2,Rd

RdAddress = IR[9:6]; // is the address of(Rd) Register (write operand)

Rs1Address = IR[13:10]; //is the address of(Rs1) Register ==> first address for read operand

Rs2Address = IR[17:14]; // is the address of(Rs2) Register ==> second address for read operand


```

// get the source and the destination registers from the register file via their addresses
Rs1 = RegisterFile[Rs1Address];
Rs2 = RegisterFile[Rs2Address];
Rd = RegisterFile[RdAddress];

// determine the control signal which will determine the second AluSrc
case (AluSrc)
2'b00: mux_2Output = Rs2;
2'b01: mux_2Output = extended_immediate16; //Output of the Extender 16
2'b10: mux_2Output = Rd;
endcase

// determine the control signal which will determine the PC Content
case (PcCont)
2'b00: PCmuxOut = sequentialPC; // pc=pc+1
2'b01: PCmuxOut = branchTargetAddress; // pc=pc+sign_ExtImm16 // this part will be done
in PC adder
2'b10: PCmuxOut = jumpTargetAddress; // pc=concatenation result
2'b11: PCmuxOut = data_memory[SP]; // pc= stack pointer

endcase

// determine the control signal which will determine the data_in to access the memory

case (DataIn)
1'b0: data_in= Rd; // ALU RESULT
1'b1: data_in= PC+1; // To push up the address of the next instruction

endcase

```

```

case (MemAdd)
    1'b0: address= outputOfALU;
    1'b1: address=  secondAddress;
endcase

case (SPorAlu2)
    1'b0: secondAddress = SP;
    1'b1: secondAddress = SPfinalResult; // either SP+1 or SP-1
endcase

case (AluSpOp)

    1'b0: SPfinalResult= SP+1;
    1'b1: SPfinalResult= SP-1;
endcase

case (Wbdata) // to determine the output of the mux in the bottom
    1'b0: toRegFile= outputOfALU;
    1'b1: toRegFile= data_out;
endcase

// Now we will check if the instruction is JMP,
    if(OpCode1==6'b001100)begin

        current_state = 4;
        jumpTargetAddress={PC[31:26],immediate26};
        PC =jumpTargetAddress;
    end

```

```

        end      // the end of JMP Instruction Decode

// Now we will check if the instruction is CALL,
    if(OpCode1==6'b001101)begin

        jumpTargetAddress={PC[31:26],immediate26};
        PC =jumpTargetAddress;

    end      // the end of CALL Instruction Decode

end // the end of Instruction Decode stage

else if (current_state == 2) begin
    // ALU STAGE === Execution

    firstOperand=Rs1;
    secondOperand= mux_2Output;

    case(AluOp1)
        2'b00: outputOfALU = firstOperand + secondOperand; // Addition
        2'b01: outputOfALU = firstOperand & secondOperand; // Bitwise AND
        2'b10: outputOfALU = firstOperand - secondOperand; // SUBTRACTION
        default: outputOfALU = 32'b0; // Default case: result is 0

    endcase

    if (outputOfALU==0)begin

```

```

        zero=1'b1; // set the zero flag if the output of the alu is zero

    end

    if (outputOfALU < 0) begin

        overflow=1'b1; // set the overflow flag if the output of alu is negative, that's mean
Rs1>Rd

    end

    // Now we will check if the instruction is BEQ
    if (OpCode1==6'b001010) begin

        if(zero == 1'b1 ) begin

            // the branch is taken and the two numbers are equal
            branchTargetAddress = PC + extended_immediate16;
            current_state = 4;
            PC=    branchTargetAddress;

        end

        else if (zero == 1'b0 ) begin

            // Branch doesnt taken
            PC=PC+1;
            current_state = 4;

```

```
end
```

```
end // the end of BEQ
```

```
// Now we will check if the instruction is BNE
```

```
if (OpCode1==6'b001011) begin
```

```
    if(zero == 1'b0 ) begin
```

```
        // the branch is taken and the two numbers are NOT equal
```

```
        branchTargetAddress = PC + extended_immediate16;
```

```
        current_state = 4;
```

```
        PC=    branchTargetAddress;
```

```
    end
```

```
else if (zero == 1'b1 ) begin
```

```
    // Branch doesnt taken
```

```
    PC=PC+1;
```

```
    current_state = 4;
```

```
end
```

```
end // the end of BNE
```

```
// Now we will check if the instruction is BGT // if Rd> Rs1 then the result of the alu is negative then overflow is 1
```

```
    if (OpCode1==6'b001000)      begin
```

```
        if(overflow == 1'b1 ) begin
```

```
            // the branch is taken and the two numbers are equal
```

```
            branchTargetAddress = PC + extended_immediate16;
```

```
            current_state = 4;
```

```
            PC=    branchTargetAddress;
```

```
        end
```

```
    else if (overflow == 1'b0 ) begin
```

```
        // Branch doesnt taken
```

```
        PC=PC+1;
```

```
        current_state = 4;
```

```
    end
```

```
end /// the end of BGT
```

```
// Now we will check if the instruction is BLT // if Rd< Rs1 then the result of the alu is positive then overflow is 0
```

```
    if (OpCode1==6'b001001)      begin
```

```
        if(overflow == 1'b0 ) begin
```

```

        // the branch is taken and the two numbers are equal
        branchTargetAddress = PC + extended_immediate16;
        current_state = 4;
        PC=    branchTargetAddress;

    end

else if (overflow == 1'b1 ) begin

    // Branch doesnt taken
    PC=PC+1;
    current_state = 4;

    end

end /// the end of BLT

end // the end of ALU stage

else if (current_state == 3) begin

    // start with load instruction and LW.POI
    if(OpCode1== 6'b00101 || OpCode1== 6'b000110 )begin

        if (Mrd && !MWr) begin

            data_memory[8]=32'h00000002;

            data_out= data_memory[outputOfALU];

```

```

end
end    // the end of load instruction

// check if the instruction is store
if (OpCode1== 6'b000111) begin
    if (!Mrd && MWr) begin

        data_memory[outputOfALU]= Rd;
        end

    end // the end of Store instruction

// here the RET instruction will be a little similar to load instruction == address from the memory
if (OpCode1== 6'b001110) begin

    if (Mrd && !MWr) begin
        PC=data_memory[SP]; // next PC is the top of the stack
        SP=SP-1; // decrement the value of SP

    end

    end // the end of RET instruction

// here we will check for the instruction CALL

    if (OpCode1== 6'b001101) begin
        if (!Mrd && MWr) begin

            SP=SP+1;

```



```

        data_memory[SP]= PC+1;
    end

end // the end of CALL instruction


// Check if the instruction is PUSH

    if (OpCode1 == 6'b001111) begin

        if (!Mrd && MWr) begin

            SP=SP+1;
            data_memory[SP]= Rd;

        end

    end // the end of PUSH


// Check if the instruction is POP
    if (OpCode1==6'b010000) begin

        Rd=data_memory[SP];
        SP=SP-1;

    end    // THE END OF POP INSTRUCTION


end // the end of MEMORY STAGE

```

```

else if (current_state == 4) begin

    if (Wbdata == 1'b0) begin
        toRegFile= outputOfALU;

    end

else if (Wbdata == 1'b1 ) begin
    toRegFile= data_out;

end

if (Wport1 ==1'b1) begin
    // we will write back the result on the register file
    RegisterFile [RdAddress]= toRegFile;
    end

else if (Wport2 == 1'b1 ) begin // so we are in the LW.POI instruction

    RegisterFile [Rs1Address]= Rs1+1;

end

PC=PC+1; // take the next instruction

end // the end of the write backStage

endmodule

```

7.2. The Test Bench For The System

```
module TestBench ();

reg clk;

reg reset;

    ///Instruction Decode Part
    wire [31:0] Rs1; // (Bus A )Output data from register 1
    wire [31:0] Rs2; // (Bus B) Output data from register 2
    wire [31:0] Rd; // Rd

    // control signals

    wire [2:0] PcCont;
    wire [2:0] Alusrc ;
    wire [2:0] AluOp1;
    wire Mrd ;
    wire MWr;
    wire Wport1;
    wire Wport2;
    wire Wbdata ;
    wire ExtOp;
    wire SPorAlu2;
    wire AluSpOp;
    wire DataIn;
    wire MemAdd;

    wire [31:0] outputOfALU;
```

```

        wire [31:0]extended_immediate16;

        wire [31:0] mux_2Output;

    wire [31:0] toRegFile; // the data will be stored in the register file

        wire [31:0] PCmuxOut;

        wire [31:0] data_out;


        multiCycleProcessor MCP (clk, reset, PcCont, ExtOp, Wport1, Wport2, Alusrc,AluOp1,MemAdd,
DataIn, Mrd, MWr, Wbdata, SPorAlu2,
        AluSpOp, Rs1,Rs2,Rd,outputOfALU, extended_immediate16);


        initial begin
            current_state = 0;

            clk = 0;

            reset = 1;

            #1ns reset = 0;

            end


            always #2ns clk = ~clk;


            initial #200ns $finish;


        endmodule

```